

**Midterm assignment (Spring 2020-2021)**  
**Computer Aided Design and Drafting Lab**  
**Section - T**  
**Marks:30**  
**Submission due date: 12/3/2021**

**Instructions:**

1. Draw the electrical circuits in AutoCad maintaining all the text visible in the circuit diagram.
2. Create PDF of AutoCad files and submit the PDF files NOT screenshot or AutoCad file.
3. Mention your group name and group members ID using text option of AutoCad.
4. Only one group member will submit the assignment file in the MStears assignment section, but all the group members should contribute while drawing





